SIMON FRASER UNIVERSITY

School of Mechatronic Systems Engineering MSE 352 Digital Logic and Microcontrollers Quiz II – Fall 2022



Student Full Name:

Student Number : Solutions


1. Use Karnaugh maps to find the minimum-cost SOP for the function:

$$f(x_1, x_2, x_3, x_4) = \overline{x_1} \overline{x_3} \overline{x_4} + x_3 x_4 + \overline{x_1} \overline{x_2} x_4 + x_1 x_2 \overline{x_3} x_4$$

assuming that there are also don't-cares defined as $D = \sum (9, 12, 14)$.

[6 marks]

2,2,+ 2,24+ 2,24+ £, £, £, £,

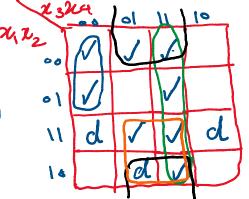

2. A 3X8 decoder is shown in the figure below. Find $f(x_0, x_1, x_2)$ in the form of Sum of minterms.

[4 marks]

approach 2: